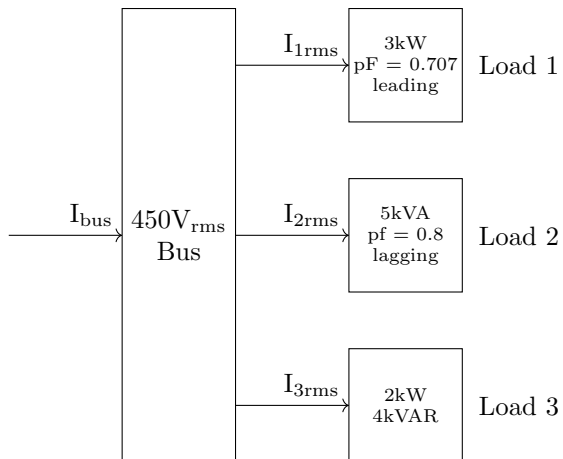


Name:

Documentation:

1. Analyze the following AC power system with three loads connected to a  $450V_{\text{rms}}$  bus.



- (a) Find the real and reactive powers for each of the 3 loads.

$P_1 =$

3kW

$Q_1 =$

-3 KVAR

$S_1 =$

4.24 kVA

$P_2 =$

4 kW

$Q_2 =$

+3 KVAR

$S_2 =$

5kVA

$P_3 =$

2kW

$Q_3 =$

4kVAR

$S_3 =$

4.47 kVA

(b) Find the total real and reactive powers supplied by the bus to the loads

$P_{\text{bus}} =$

9 kW

$Q_{\text{bus}} =$

4 kVAR

(c) Find the bus apparent power.

$S_{\text{bus}} =$

9.85 kVA

(d) Find the RMS value of the bus current.

$I_{\text{bus}} =$

21.9 Arms

2. A 3HP induction motor is powered from a  $220V_{\text{rms}}$  bus. While delivering rated power, it operates at 80% efficiency and 0.85 power factor (lagging).

(a) Find the real mechanical power out in Watts.

$$P_{\text{mech}} =$$

2.24 kW

(b) Find the real electrical power into the motor.

$$P =$$

2.80 kW

(c) Find the apparent power of the motor

$$S_{\text{motor}} =$$

3.29 kVA

(d) Find the reactive power of the motor.

$$Q_{\text{motor}} =$$

1.73 kVAR

(e) Find the current drawn by the motor from the  $220V_{\text{rms}}$  bus

$$I_{\text{motor}} =$$

15.0 A rms

- (f) We wish to reduce this current to 13A by attaching a second item to the  $220V_{\text{rms}}$  bus that has only a negative reactive power. Determine the amount of that reactive power.

 $Q_{\text{device}} =$  $-1.14 \text{ kVAR}$