

ECE 215

Practice problems

1. Convert and plot all of these values on the complex plane

a. Convert to rectangular:

i. $10\angle -10^\circ$

ii. $5\angle 160^\circ$

iii. $7\angle 50^\circ$

b. Convert to phasor

i. $-10 + j6$

ii. $5 - j6$

iii. $-17 - j4$

ECE 215

2. Perform the requested mathematical operation:

1. $(10+j5)+(-4-j16)$

2. $(10+j5)*(-4-j16)$

3. $\frac{12\angle 15^\circ}{3\angle 27^\circ}$

4. $12\angle 150^\circ + 6\angle 27^\circ$

5. $5\angle 57^\circ * 6\angle 36^\circ$

ECE 215

3. Perform the following computations, preferably by hand. (Use your calculator to check your answers.)

a. $(j6)(j3)$

b. $j5 + 5 + j8 + 7$

c. $\frac{j18}{j3}$

d. $(8 + j6)(j8 + 2)$

e. $\frac{1}{8+j5} + \frac{1}{8+j7}$

4. Convert your answers from Problem 3 above to phasor notation

a.

b.

c.

d.

e.

ECE 215

5. Convert the following from phasor notation to rectangular coordinates:

a. $6\angle 30^\circ$

b. $2\angle 90^\circ$

c. $18\angle 45^\circ$

d. $7\angle 54^\circ$

6. Perform the following calculations:

a. $(6\angle 30^\circ)(2\angle 90^\circ)$

b. $\frac{2\angle 90^\circ}{6\angle 30^\circ}$

c. $6\angle 30^\circ + 2\angle 90^\circ$

d. $2\angle 90^\circ - 6\angle 30^\circ$

e. $\frac{6\angle 30^\circ}{3\angle 90^\circ}$

ECE 215

7. Convert the following values into impedances:

a. $C = 10\mu\text{F}$, $f = 200\text{ Hz}$

b. $L = 20\text{ mH}$, $f = 20\text{ Hz}$

c. $R = 15\Omega$, $f = 100\text{ Hz}$

8. In a given circuit, if $v_s(t) = 100\cos(360^\circ 1kt)\text{V}$, determine the impedances of the following components:

a. $R = 100\ \Omega$

b. $C = 66\ \mu\text{F}$

c. $L = 10\text{ mH}$

9. In a given circuit, if $v_s(t) = 100\cos(360^\circ 500t)\text{V}$, determine the impedances of the following components:

a. $R = 150\ \Omega$

b. $C = 270\ \mu\text{F}$

c. $L = 144\text{ mH}$

10. Convert the voltage source values to phasor RMS values


ECE 215

a. $v_s(t) = 5 \cos(360^\circ * 100 * t) V$


b. $v_s(t) = 377 \cos(360^\circ * 60k * t + 30^\circ) V$

c. $v_s(t) = 169.73 \cos(360^\circ * 400 * t - 45^\circ) V$

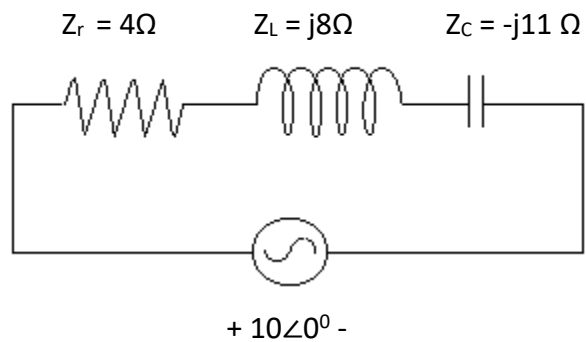11. For the circuit below, determine the equivalent impedance. Then write a voltage divider equation to determine the voltage drop over the inductor.




12. The circuit below is operating at 400 Hz. Determine the equivalent impedance. What is the voltage and current drop over each component when $V_S = 150V\angle 0^\circ$, $R = 1k\Omega$, $L = 30\text{ mH}$, and $C = 20\text{ }\mu\text{F}$? Also, find I_S without using Z_{eq}

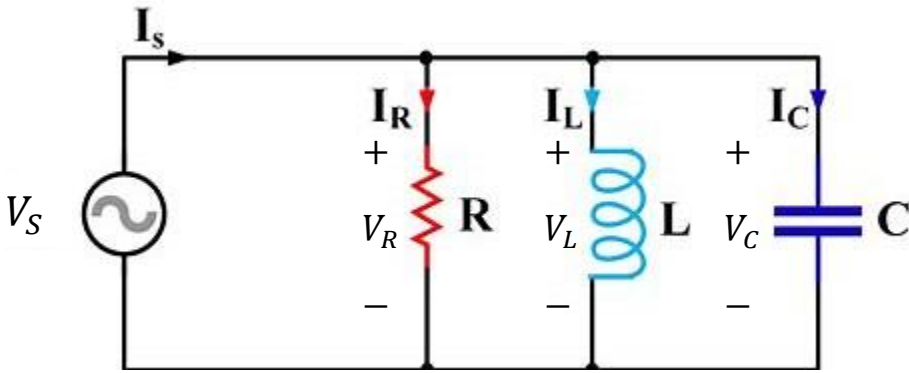


ECE 215

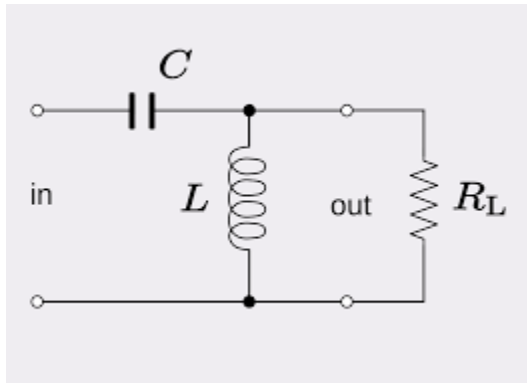13. For the circuit below, determine the equivalent impedance, given the input frequency is 2kHz, $L = 27\text{mH}$, $C = 150\text{nF}$, and $R = 5\text{k}\Omega$




14. For the circuit below, determine the equivalent impedance, given the input frequency is 60Hz, $R = 20\ \Omega$, $C = 15\text{nF}$, and $L = 2\text{mH}$. (Assume the voltage source is AC despite the DC source symbol.)

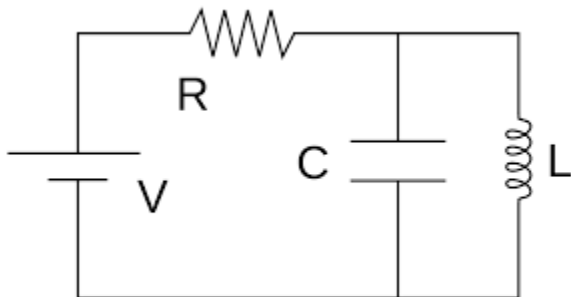

ECE 215

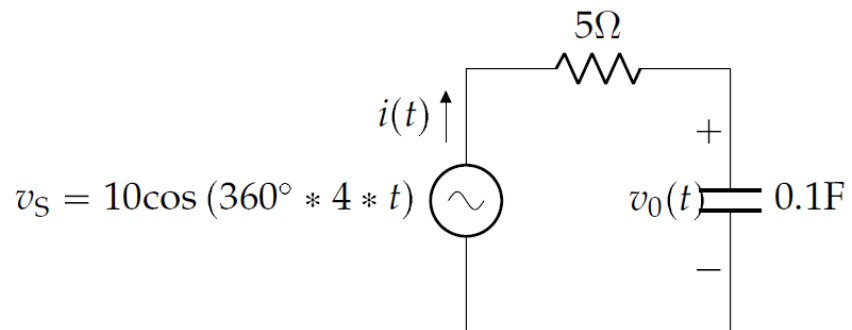15. For the circuit below, find $v_0(t)$ and $i(t)$



16. For the circuit below, find \tilde{V}_o and the current flowing through the capacitor

