 



# Finite State Machines

Structured two ways:

1. Moore machine



2. Mealy machine

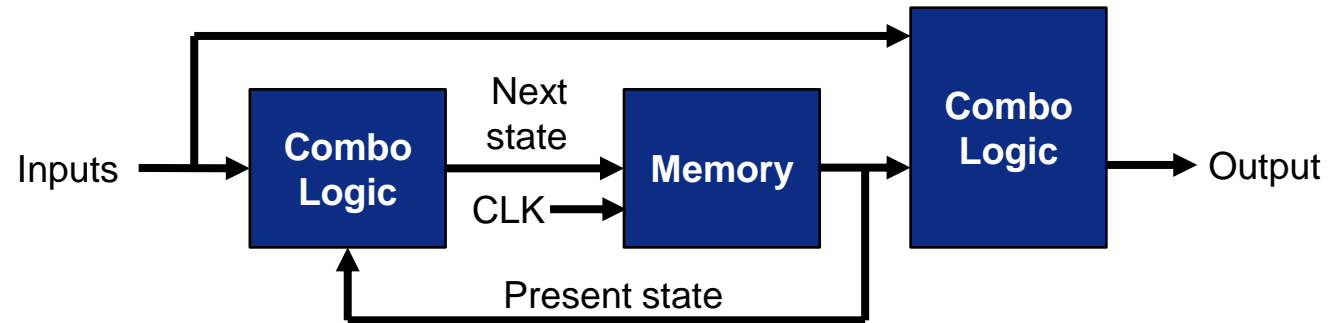


**Modern FSM designs use Field Programmable Gate Arrays (FPGAs) which are programmed using VHDL or Verilog**


# State Transition Diagrams

- Model FSMs using **state transition diagrams**
- These consist of:
  1. : all possible configurations of a system
  2. : connections between states
  3. : actions that trigger a transition

Moore machine example:

 


Mealy machine example:

 

# State Transition Diagrams

Example 1: Design a Moore FSM to recognize the binary sequence '10'.

Output = 0:  
1:

 

Meaning  
of states:

S0  
elements of  
sequence  
observed

S1  
element  
observed

S2  
observed

# State Transition Diagrams

---

## Process for developing a solution:

1. Define/                    the states (binary representation)  
                                 /encode the input(s)
3. Define/encode the
4. Create a state transition
5. Create a                    mapping present state/input to the                    and
6. Express                    and                    as logic equations of the present states  
and
7. Implement with the required                    and

# State Transition Diagrams

1. 3 states, so need 2 bits

$$2^{\text{bits}} = \text{max \# of states} \rightarrow 2^2 = 4 \text{ states}$$

$$S0 = 00$$

$$S1 = 01$$

$$S2 = 10$$


2. Input is already binary,  $x = 0$  or  $1$

(what if it was  $x = 1, 2, 3, 4$ ?)

3. Define/encode outputs

4. Create the state transition diagram – done!

5. Create the table

 

Present State		Input	Next State		Output
$q_1$	$q_0$	$x$	$q_1^+$	$q_0^+$	$z$
0	0	0			
0	0	1			
0	1	0			
0	1	1			
1	0	0			
1	0	1			
1	1	0			
1	1	1			


# State Transition Diagrams

6. Create combinational logic for  $q_1^+$ ,  $q_0^+$ , and  $z$   
 ■ Use SOP or POS based on situation

$q_1^+ =$

$q_0^+ =$


$z =$

 

Present State		Input	Next State		Output
$q_1$	$q_0$	$x$	$q_1^+$	$q_0^+$	$z$
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	1	0	0
0	1	1	0	1	0
1	0	0	0	0	1
1	0	1	0	1	1
1	1	0	x	x	x
1	1	1	x	x	x
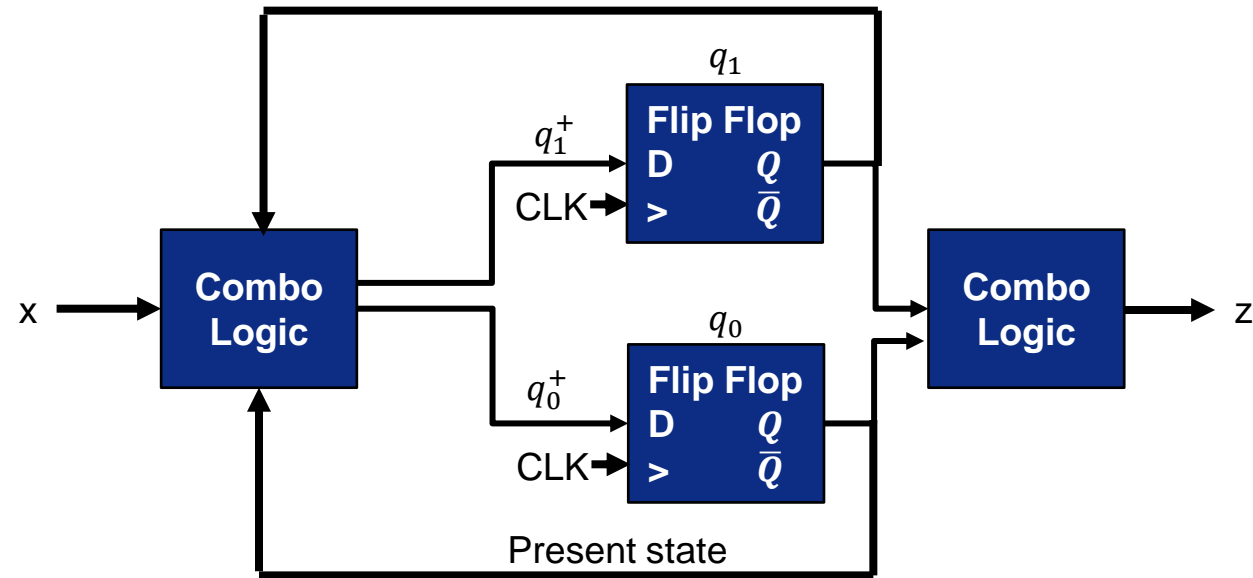
# State Transition Diagrams


- Implement with the required flip flop memory and logic gates



The D flip flop will pass its input to the output (Q) on either the rising edge or falling edge of the CLK.
 
# State Transition Diagrams

- What would be an equivalent Mealy diagram?



Meaning  
of states:

S0  
 elements of  
 sequence  
 observed

S1  
 element  
 observed


Present	Input	Next	Output
$q_0$	$x$	$q_0^+$	$z$
0	0	0	0
0	1	1	0
1	0	0	1
1	1	1	0

Mealy implementation *could* have fewer states and use less area. However, a Moore implementation is generally “safer”.


 
# Example 2

- Implement a 2-bit counter from 0 to 3 that will count up when it receives a '1' and holds the value when it receives a '0'
  - How many states? **4** How many bits?  **$4=2^2 \rightarrow 2$  bits**



Present State		Input	Next State		Output	
$q_1$	$q_0$		$q_1^+$	$q_0^+$	$z_1$	$z_0$
0	0	0				
0	0	1				
0	1	0				
0	1	1				
1	0	0				
1	0	1				
1	1	0				
1	1	1				

$q_1^+ =$

$z_1 =$

$z_0 =$

\* Output = state, so this is a **machine**      \* Same implementation idea as in previous example

## Example 3

- A vending machine requires 20¢ to dispense. You can enter a N = nickel, D = dime, or Q = quarter and then get change. For change you can only get a nickel, a dime, or a nickel and a dime. All other additional change is credited. Design the FSM.


1. What are the states?
2. What are the inputs?
3. What are the outputs?



# Example 3

- A vending machine requires 20¢ to dispense. You can enter a N = nickel, D = dime, or Q = quarter and then get change. For change you can only get a nickel, a dime, or a nickel and a dime. All other additional change is credited. Design the FSM.

 4. Create a state transition diagram:      INPUT/OUTPUT =   Insert / Dispense   Return   Return



# Example 3

- A vending machine requires 20¢ to dispense. You can enter a N = nickel, D = dime, or Q = quarter and then get change. For change you can only get a nickel, a dime, or a nickel and a dime. All other additional change is credited. Design the FSM.

5. Create a state transition table


... we'll skip Steps 6-7.

	Present State		Input		Next State		Output		
	$q_1$	$q_0$	$x_1$	$x_2$	$q_1^+$	$q_0^+$	$z_2$	$z_1$	$z_0$
0	0	0	0	0					
1	0	0	0	1					
2	0	0	1	0					
3	0	0	1	1					
4	0	1	0	0					
5	0	1	0	1					
6	0	1	1	0					
7	0	1	1	1					
8	1	0	0	0					
9	1	0	0	1					
10	1	0	1	0					
11	1	0	1	1					
12	1	1	0	0					
13	1	1	0	1					
14	1	1	1	0					
15	1	1	1	1					

# Example 4

- Example: We need to design an FSM for a traffic light intersection with sensors that tell us:

Input - X	
00	No traffic
01	N-S traffic
10	E-W traffic
11	Both traffic

 


- We want N-S to stay green if there is No traffic or N-S traffic (reassess every 5 seconds)
- Otherwise, we want to transition to Yellow for 1 sec
- Then go to N-S red and E-W green and stay if there is E-W traffic (reassess every 5 seconds)
- Otherwise transition to yellow for 1 sec
- Then go to N-S green and E-W red
- Repeat

# Example 4

- Example: We need to design an FSM for a traffic light intersection with sensors that tell us:

Input - X	
00	No traffic
01	N-S traffic
10	E-W traffic
11	Both traffic

 

States	
S0 – 00	NS green, EW red
S1 – 01	NS yellow, EW red
S2 – 10	NS red, EW green
S3 – 11	NS red, EW yellow


- Step 1: Define/encode the states.
  - Need 4 states
- Steps 2-3: Define/encode the inputs and outputs
  - Outputs are the states (so... Moore or Mealy?)

# Example 4


- Example: We need to design an FSM for a traffic light intersection with sensors that tell us:

Input - X	
00	No traffic
01	N-S traffic
10	E-W traffic
11	Both traffic

States	
S0 – 00	NS green, EW red, Delay 5s
S1 – 01	NS yellow, EW red, Delay 1s
S2 – 10	NS red, EW green, Delay 5s
S3 – 11	NS red, EW yellow, Delay 1s

 

 - Step 4: Create State Transition Diagram



# Example 4

- Step 5: Create State Transition Table
- Step 6: Express next states and outputs as expressions of the present states and inputs.

$$q_1^+ =$$

$$q_0^+ =$$

	Present State		Input		Next State		Output	
	$q_1$	$q_0$	$x_1$	$x_0$	$q_1^+$	$q_0^+$	$z_1$	$z_0$
0	0	0	0	0				
1	0	0	0	1				
2	0	0	1	0				
3	0	0	1	1				
4	0	1	0	0				
5	0	1	0	1				
6	0	1	1	0				
7	0	1	1	1				
8	1	0	0	0				
9	1	0	0	1				
10	1	0	1	0				
11	1	0	1	1				
12	1	1	0	0				
13	1	1	0	1				
14	1	1	1	0				
15	1	1	1	1				



# Example 4

- Step 7: Implement with gates and flip flops
  - Drawing the logic gates for the combo logic will get messy fast, so we'll just go with "Combo Logic" boxes representing all of it.

