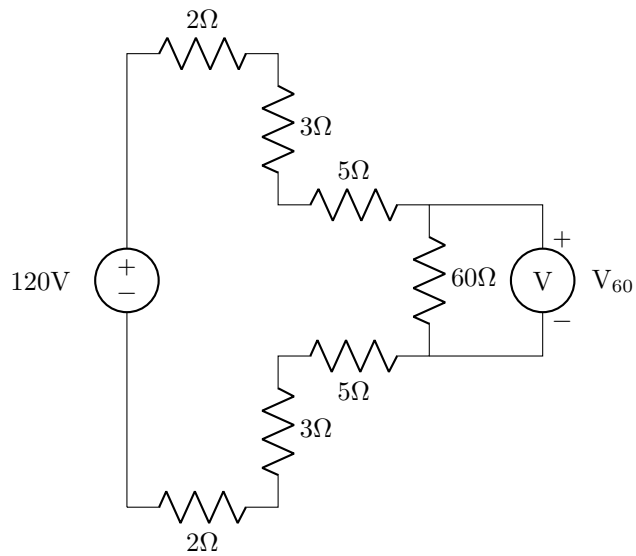


1. Analyze the following circuit:



(a) What power does the source supply?

$P_s =$


180 W

(b) What does the voltmeter read?

$V_{60} =$

90.0 V

2. Analyze the following circuit:

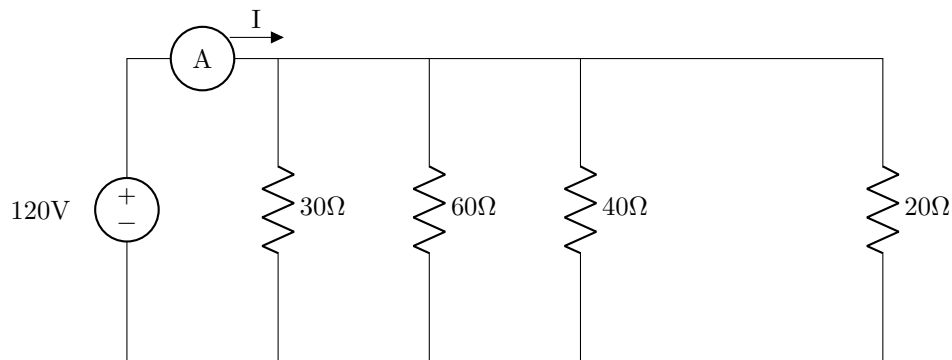

(a) Find the current through and power absorbed by each resistor.

$I_{30} =$

4.00 A

$P_{30} =$

480 W

$I_{40} =$

3.00 A

$P_{40} =$

360 W

$I_{60} =$

2.00 A

$P_{60} =$

240 W

$I_{20} =$

6.00 A

$P_{20} =$


720 W

(b) What does the ideal ammeter read?

$I =$

15.0 A

3. Given the following 4-band resistor:

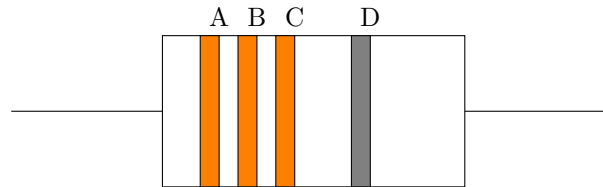

(a) What is the nominal resistance value? What would be the maximum possible resistance value (at the edge of maximum tolerance)?

$R_{\text{nominal}} =$

33.0 k Ω

$R_{\text{max}} =$

36.3 k Ω

(b) What would be the bands for a 150 Ω resistor with 20% tolerance?

band 1 =

Brown

band 2 =

green

band 3 =

Brown

band 4 =

none

4. Given that the power absorbed by a resistor is $P = \frac{V^2}{R} = I^2 R$:

(a) How much voltage can you put across a 220 Ω , 1W resistor?

$V =$

14.8V

(b) How much current can you put through a 100 Ω , 2W resistor?

$I =$

141mA