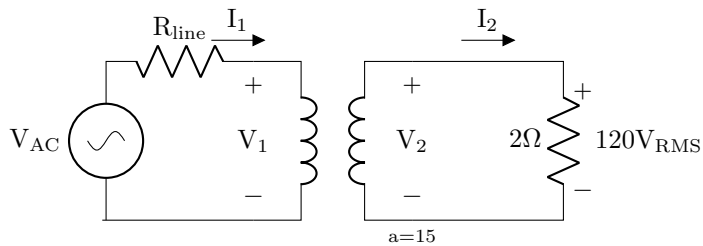


Name:

Documentation:

1. Given the following AC power system with an ideal transformer, with a load resistance of $R_{\text{load}} = 2\Omega$, a turns ratio of $a = 15$, and a $R_{\text{line}} = 36.49\Omega$, answer the following questions:



- (a) If we desire the load voltage to be $120V_{\text{rms}}$, find the load power and the load current. Since this is a resistor, use real power.

$$P_{\text{load}} =$$

$$7.20 \text{ kW}$$

$$I_{\text{load}} =$$

$$60.0 \text{ A}$$

- (b) Find the voltage and current required on the primary (1) side of the transformer.

$$V_1 =$$

$$1.80 \text{ kV}$$

$$I_1 =$$

$$4.00 \text{ A}$$

- (c) Determine the system efficiency.

$$\eta =$$

$$92.5\%$$

- (d) Use KVL to establish the required source voltage.

$$V_s =$$

$$1.95 \text{ kV}$$

2. Assume you want to increase the transmission efficiency of Problem 1 to 97.5% by decreasing R_{line} , find the required value.

$R_{\text{line}} =$


$11.54 \, \Omega$

3. Assume you want to increase the transmission efficiency of Problem 1 again to 97.5%, this time by changing the turns ratio, a . Find the new turns ratio.

$a =$

26.67

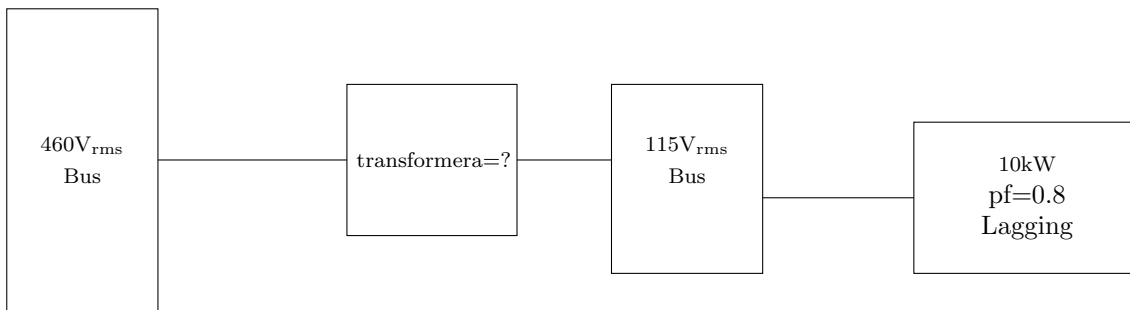4. Analyze the following power delivery system.



(a) Find the transformer turns ratio (a).

$a =$

4

(b) Find the RMS current drawn from the 115V_{rms} bus, then determine the corresponding current drawn from the 460V_{rms} bus.

$I_{115} =$

109 A

$I_{460} =$

27.2 A