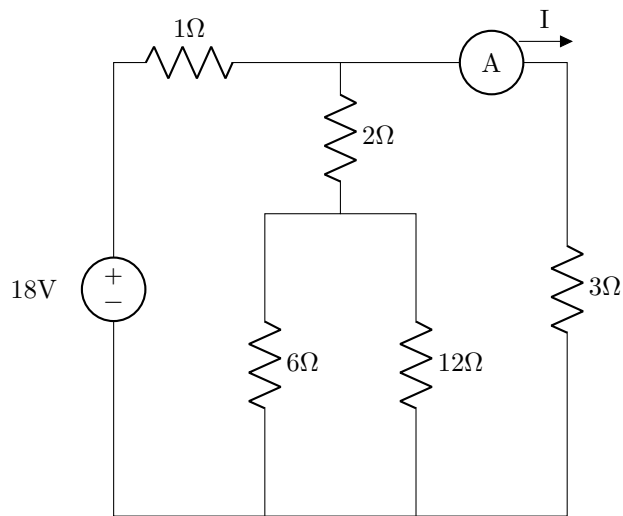


1. Analyze the following circuit:



(a) What does the ideal anmmeter read?

$I =$


(b) What power is consumed by the 12Ω resistor?

$P_{12} =$

(c) If you want to protect the 18V source from abnormal circuit conditions, suggest a rated value for a fuse to be placed in series with the source.

fuse =

2. Analyze the following circuit:

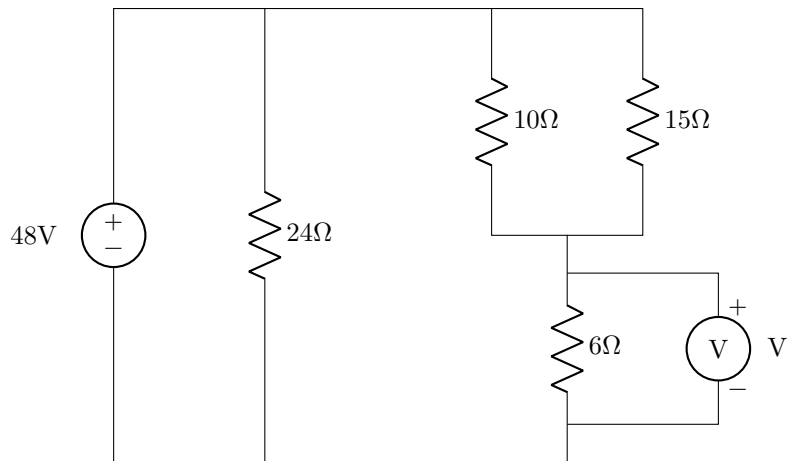


(a) Find the power absorbed by the 10Ω resistor.

$P_{10} =$

(b) What does the ideal voltmeter read?

$V =$

3. Analyze the following circuit:

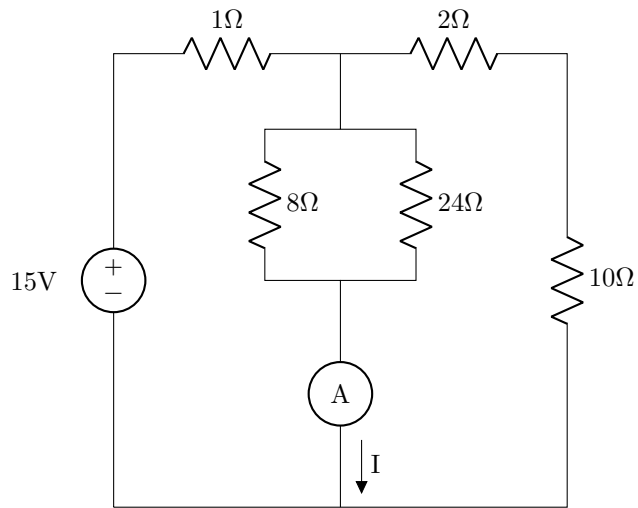

(a) Find the power absorbed by the 10Ω resistor.

$P_{10} =$

(b) What does the ideal ammeter read?

$I =$

(c) Suggest a fuse rating to protect the 15V source.

$I =$