

ECE 215 Spring 2025

Objective 1.2:
Circuit Protection




UNITED STATES
AIR FORCE
ACADEMY

Objective 1.2

I can determine appropriate circuit breaker values for adequate system protection.

DON'T LET THE SMOKE OUT!

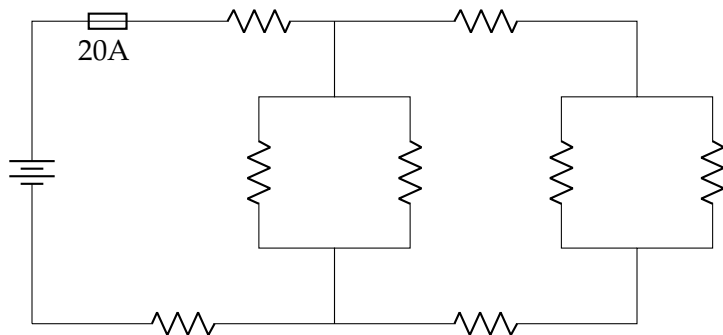


Considerations:

- Are the components protected from failures?
- Are the load voltages/currents within operational limits?
- → We need to analyze the circuit!

METHOD


- Label nodes
- Combine resistors working towards source
- Find source current
- Choose appropriate circuit protection
 - Select circuit protection rated for current between 10% and 50% higher than source current

EXAMPLE - FIND I_s AND SELECT FUSE

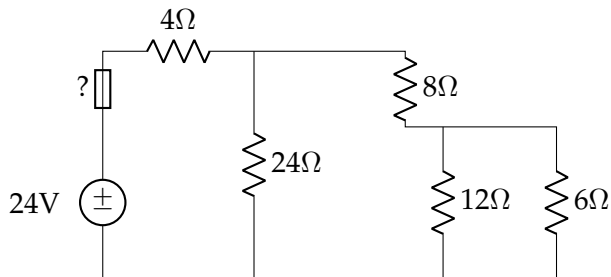

Rating
2A
2.5A
3A
3.5A
4A

FIND I_S AND SELECT FUSE???

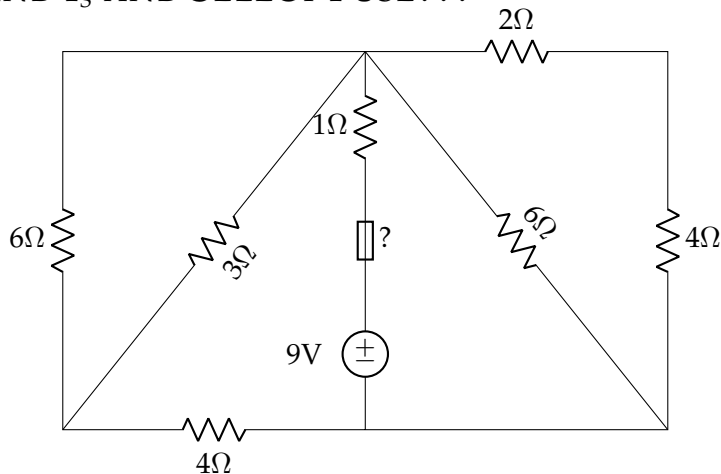

METHOD

1. Replace fuse with a short circuit (wire), label nodes
2. Start with source, label nodes on either side, and at **minor** nodes (2 components) draw downward
3. At **major** node (more than 2 components), draw horizontal line & hang components off these. Cross off components as you've redrawn them.
4. Analyze as before!