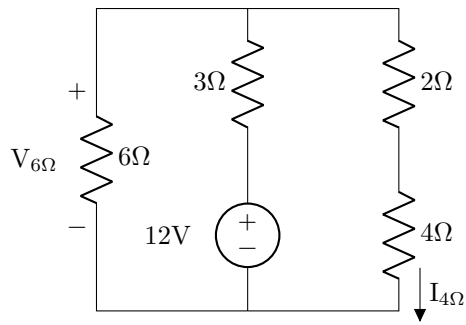


1. Analyze the following circuit:



(a) Find  $I_{4\Omega}$

$I_{4\Omega} =$


(b) Find  $V_{6\Omega}$

$V_{6\Omega} =$

(c) Find the power delivered by the source.

$P_s =$

2. Analyze the following circuit:

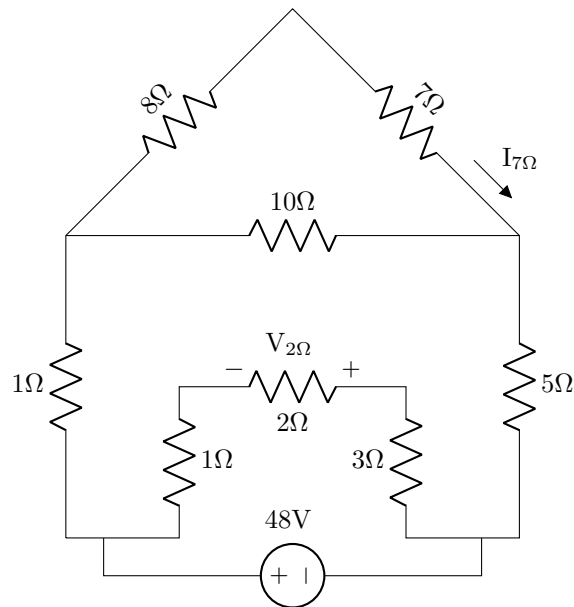

(a) Find  $V_{2\Omega}$  and  $I_{7\Omega}$ .


$V_{2\Omega} =$

$I_{7\Omega} =$

(b) What equivalent resistance does the 48V source “see”?

$R_{eq} =$

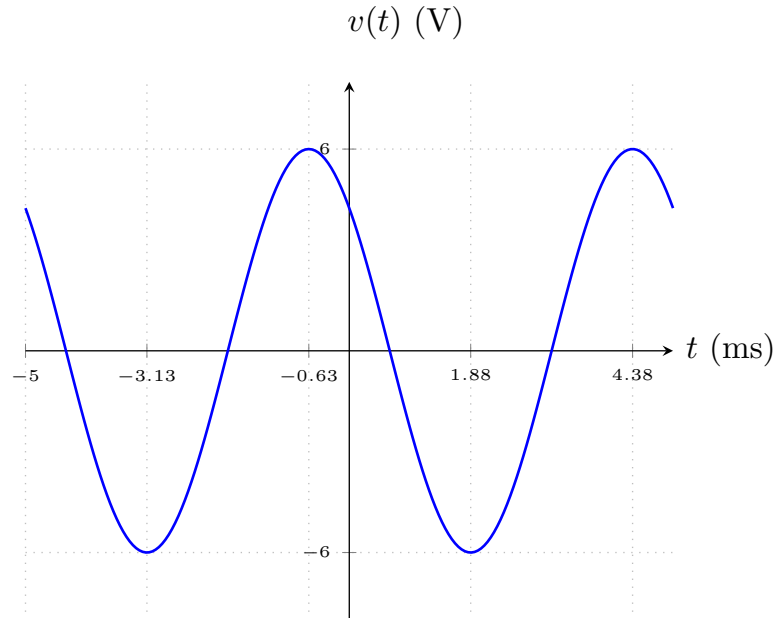3. Given the following sinusoidal waveform:



(a) Find its period and frequency in Hz (pay attention to the scaling).

T =

f =


(b) What is its RMS value?

$V_{\text{RMS}}$  =

(c) Write an expression for this signal in the form of  $V_{\text{pk}} \cos(\omega t + \phi_{\text{rad}})$

$V(t) =$

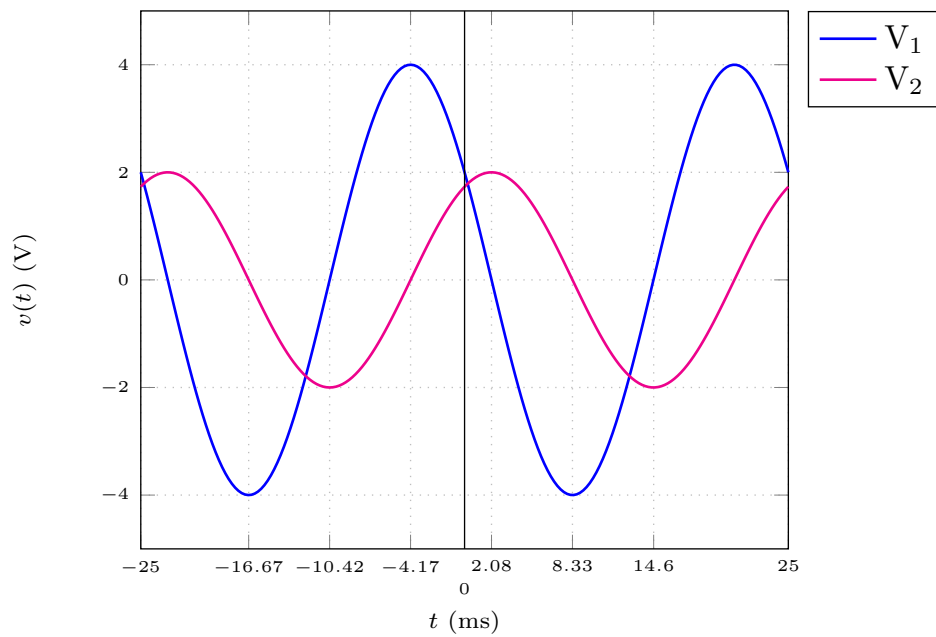4. Given the following two sinusoidal waveforms, which are at the same frequency:



(a) Find its period and frequency in Hz (pay attention to the scaling).

$T =$

$f =$

(b) What is its RMS amplitude of each signal?


$V_1 =$

$V_2 =$

(c) Which signal leads, and by how many **degrees**?

Answer =

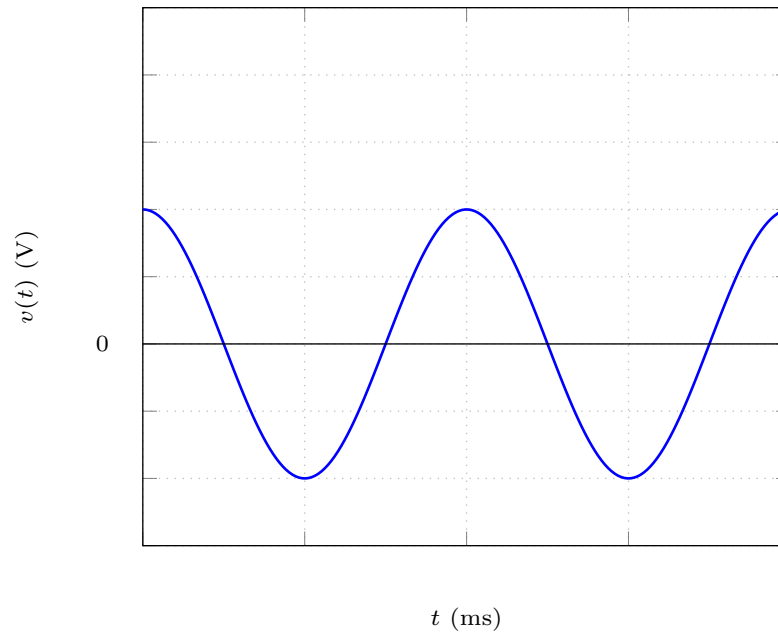5. Given the following oscilloscope waveform, where the vertical scale is set to 5V /div and the horizontal axis is set to 1ms/div:



- (a) Compute the frequency in Hz.

$f =$

- (b) Compute the RMS amplitude.

$V_{\text{RMS}} =$